
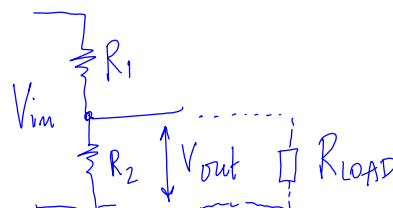
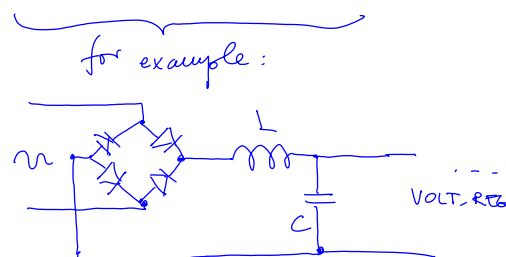


EE 444/645: Embedded Systems Design



Voltage Regulators

Spring 2023. Set: **8**


Instructor: Dr. Dejan Raskovic

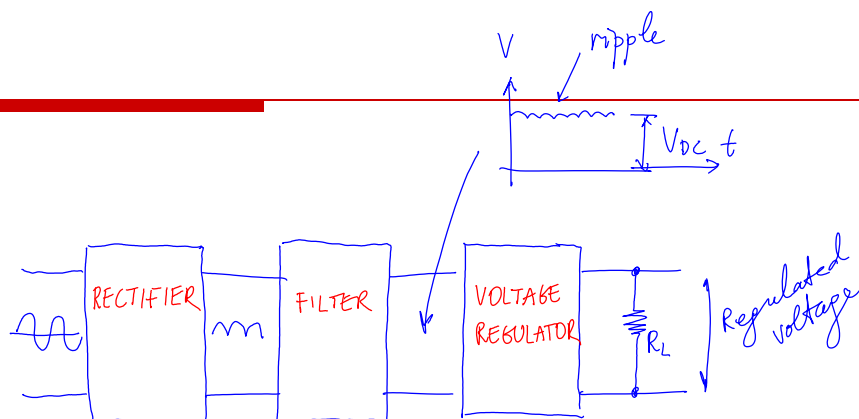


Linear voltage regulators

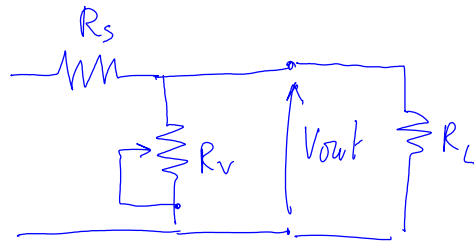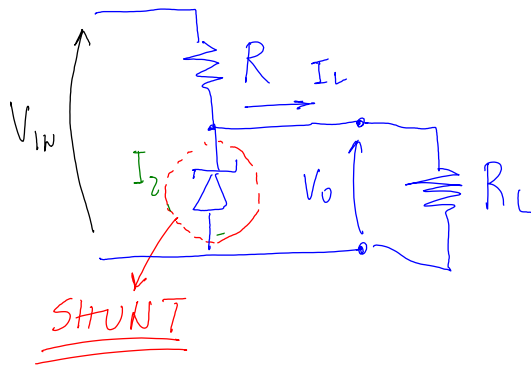


Linear series voltage regulators

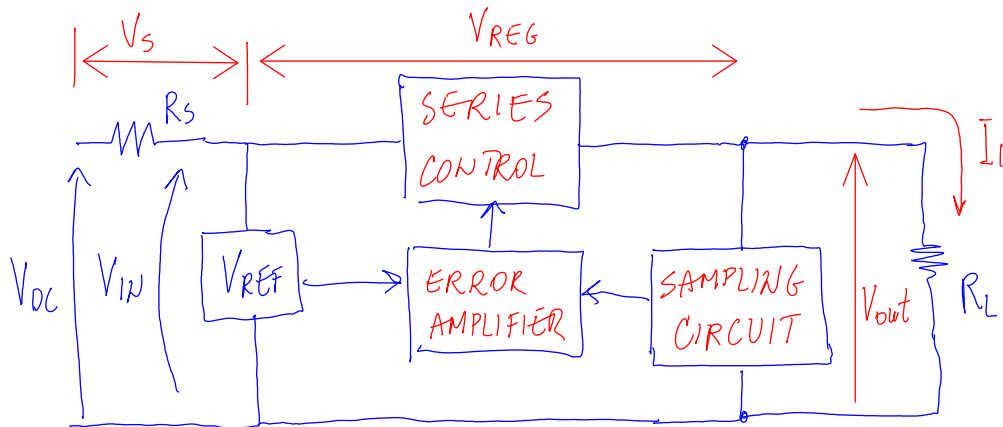


Linear series voltage regulators

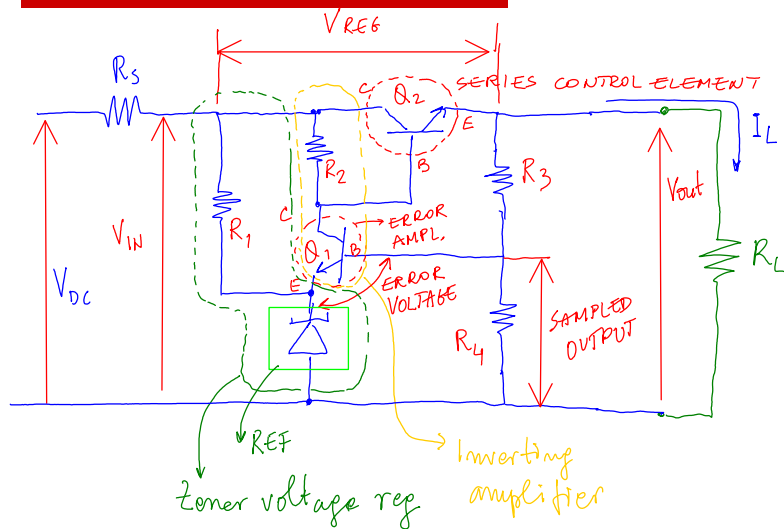

Switching regulators

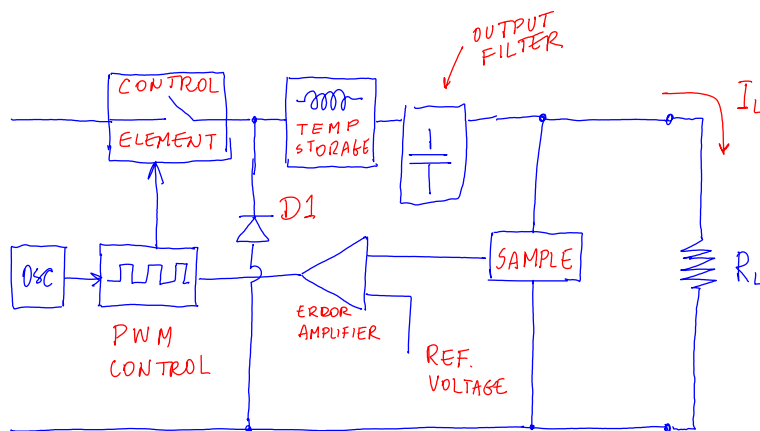


Regulation

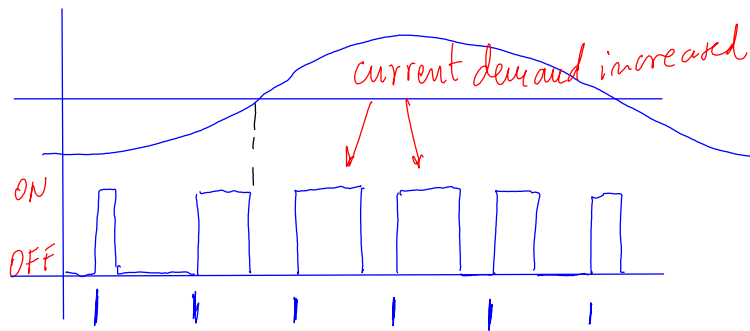


Keep the grounds separated


Boost (step-up) converter

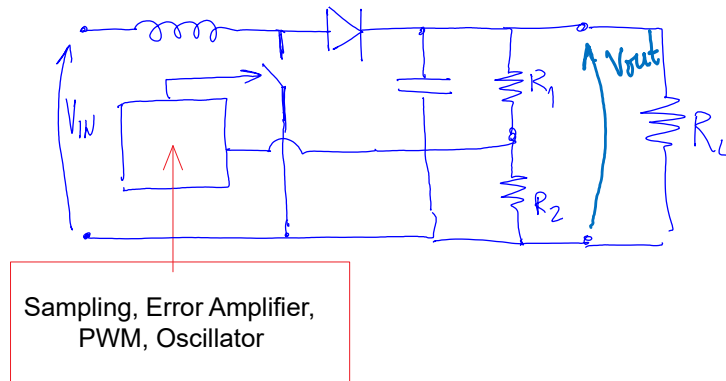

Buck

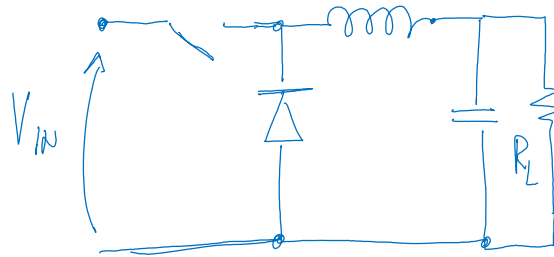

Charge pump

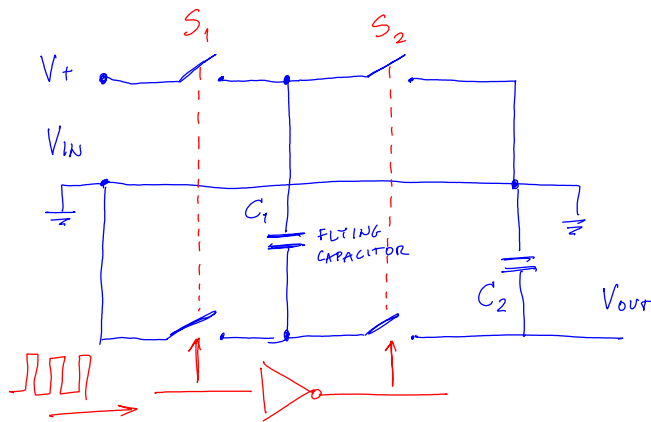

This one is inverting voltage.

Charge pump

From: Palumbo and Pappalardo, "Charge Pump Circuits:...", *IEEE Circuits and Systems Magazine*, First Quarter 2010, pp. 31-45

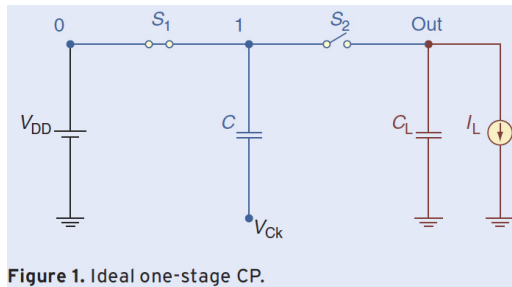


Figure 1. Ideal one-stage CP.

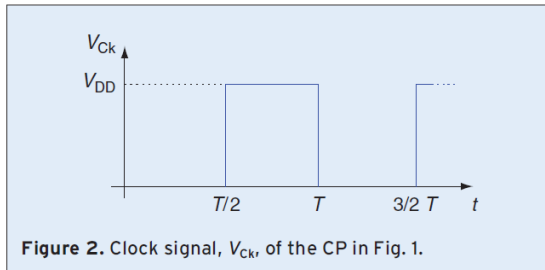


Figure 2. Clock signal, V_{ck} , of the CP in Fig. 1.

$$V_{Out}|_{\text{Steady State}} = 2V_{DD} - \frac{I_L \cdot T}{C}$$

For an n-stage CP:

$$V_{Out}|_{\text{Steady State}} = (N + 1)V_{DD} - N \frac{I_L \cdot T}{C}$$

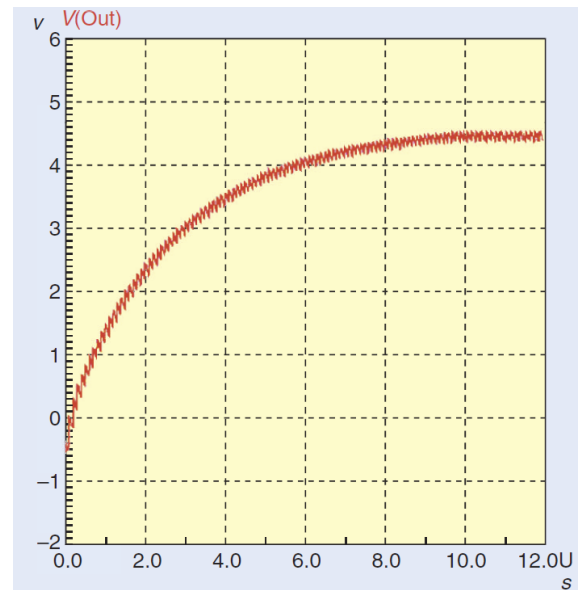


Figure 4. Output voltage of the one stage charge pump.

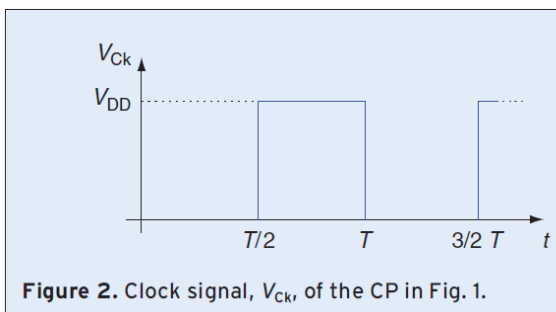


Figure 2. Clock signal, V_{ck} , of the CP in Fig. 1.


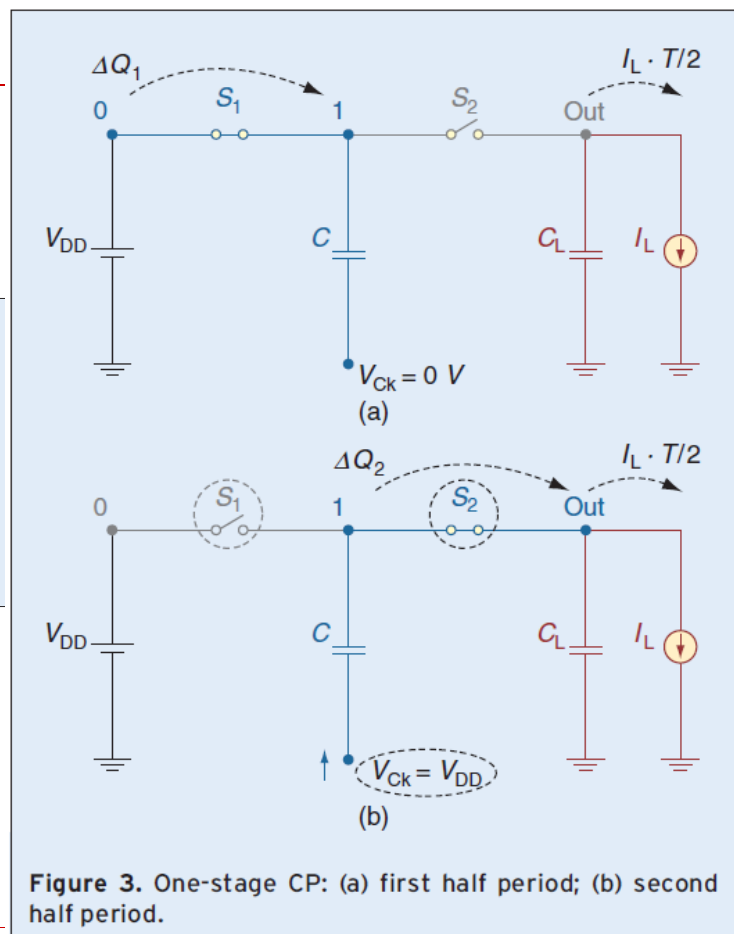
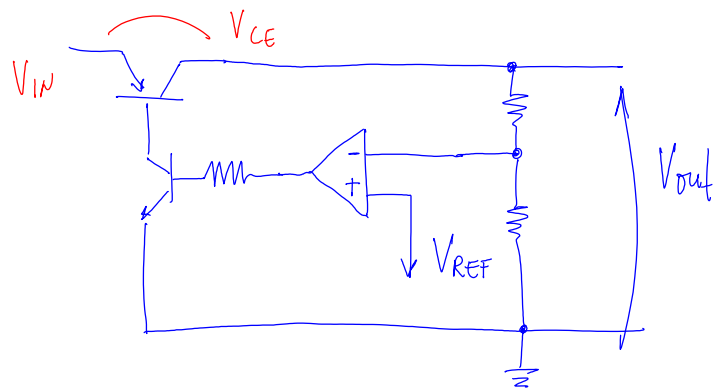


Figure 3. One-stage CP: (a) first half period; (b) second half period.

Low Dropout Regulator (LDO)

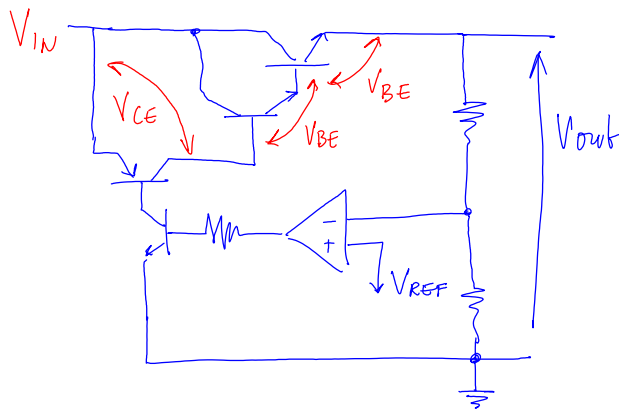

PROs and CONs of linear/switching VRs

Linear

- PRO: low output noise
- PRO: fast response to changes in V_{in}/V_{out}
- PRO: at our power levels – usually smaller and cheaper
- CON: inefficient (can be as bad as 30%-50%, be careful when selecting)
- CON: acoustic noise
- CON: **can't boost voltage**
- ...

Switching


- PRO: more efficient
- PRO: Can boost voltage
- CON: switching noise (RFI)
- ...

When you can't make up your mind...

- ☐ Three buck VRs
- ☐ Three LDO linear VRs
- ☐ A Buck-boost regulator
- ☐ Li-Ion Battery charger
- ☐ Two Load Switches
- ☐ Up to 7 regulated voltages
- ☐ All programmable through I²C

TOP VIEW
(BUMP SIDE DOWN)

MAX20345

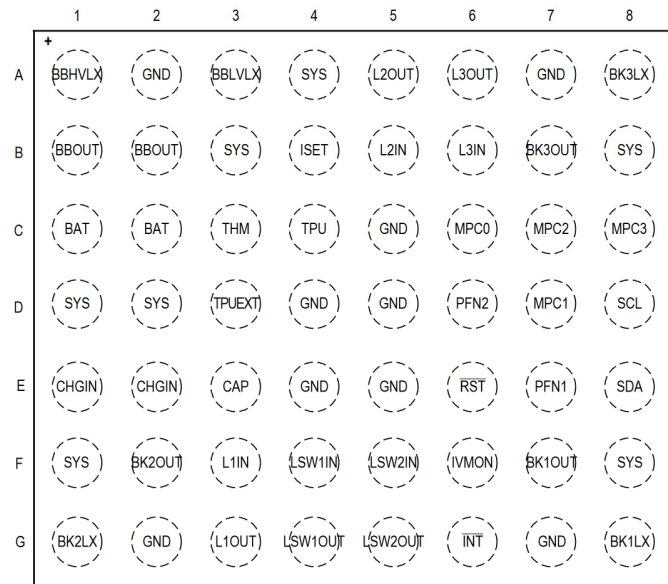

56 WLP
(3.37mm x 3.05mm)